

---

# Lattice VHDL Training

## Part I

---


# VHDL

## Basic Modeling Structure

# VHDL Design Description


- VHDL language describes a digital system as a set of modular blocks. Each modular block is described by a pair of **entity** and **architecture**.

<code>entity counter</code>	<code>architecture counter_design of counter</code>
<code>.... ....</code>	<code>.... ....</code>
<code>end counter;</code>	<code>end counter_design;</code>
<code>entity tff</code>	<code>architecture tff_design of tff is</code>
<code>.... ....</code>	<code>.... ....</code>
<code>end tff;</code>	<code>end tff;</code>
<code>entity inv</code>	<code>architecture inv_design of inv</code>
<code>.... ....</code>	<code>.... ....</code>
<code>end inv;</code>	<code>end inv_design;</code>
<code>entity dff</code>	<code>architecture dff_design of dff is</code>
<code>.... ....</code>	<code>.... ....</code>
<code>end dff;</code>	<code>end dff;</code>

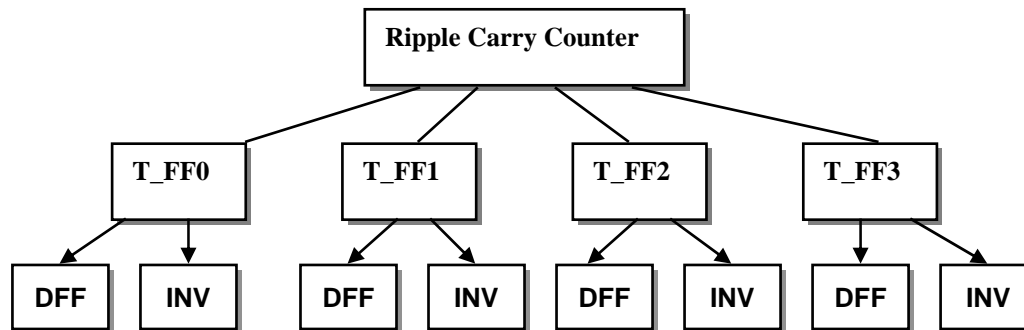
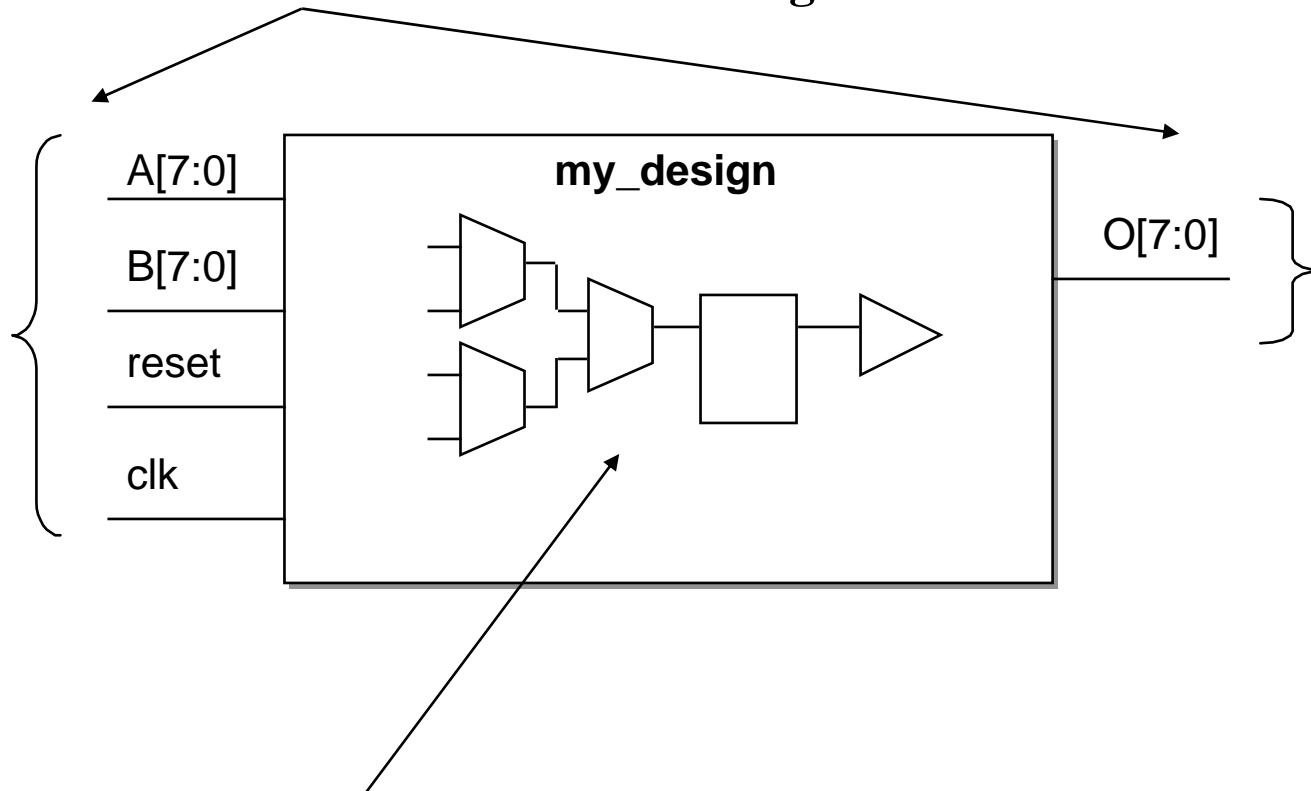
# VHDL Design Descriptions

- VHDL design description consist of an ENTITY and ARCHITECTURE pair
  - The **ENTITY** describes the **design I/Os**




- The **ARCHITECTURE** describes the **content of the design**

# The Entity - example

---

- VHDL description of the entity:

 
```
ENTITY black_box is  
    port ( rst : IN std_logic;  
          clk : IN std_logic;  
          d   : IN std_logic_vector (7 downto 0);  
          q   : BUFFER std_logic_vector (7 downto 0);  
          co  : OUT std_logic );  
END black_box;
```



- Note: VHDL is **NOT** case sensitive!

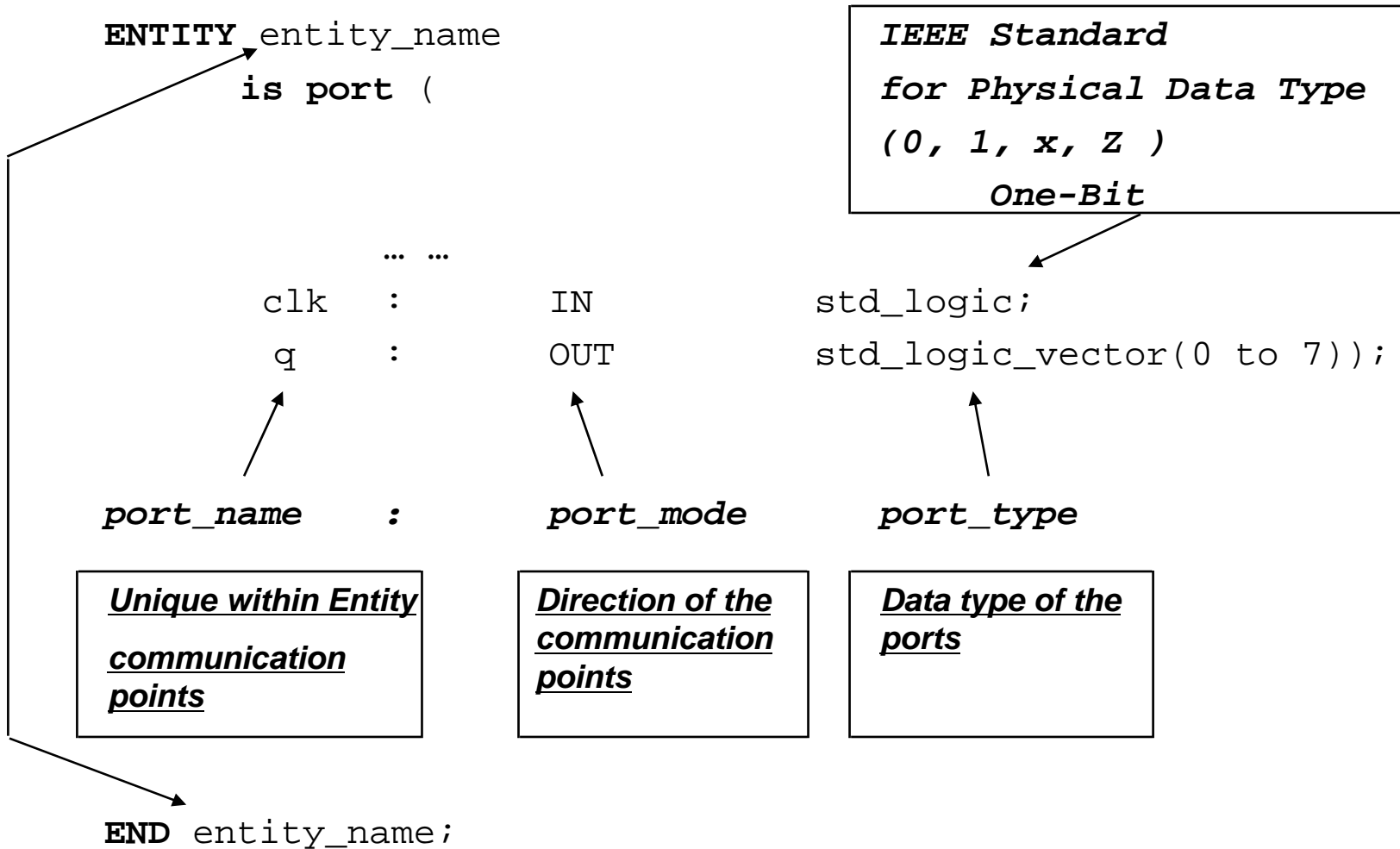
# The Entity - General Format for Port Declaration

- Entity only describes the circuit interface but not function




# PORT Modes


---

 

- IN

 


- OUT

 


- OUT

(Tri-State)

 

- INOUT

 

- Buffer

# PORT Types

---

- **integer** Useful as index holders for loops and constants. When used for I/O signals, usually reference counters
- **Boolean** Can take values of 'TRUE' and 'FALSE'
- **std\_logic** Standard industry logic type, has values of '0', '1', 'X', and 'Z' defined by IEEE std 1164.
- **std\_logic\_vector** A grouping of std\_logic, standard industry logic type



# PORT Types

- VHDL is a strongly typed language. You cannot assign one signal type to another signal type.


**ENTITY** example **is**

```
port (Q1 : OUT Integer; ...  
      Q2 : OUT std_logic_vector( 3 downto 0));
```


**END** example;

**Architecture** behavior **of** example **is**

**begin**

 

 -- Q2 is declared in 4 bit std logic vector type



```
Q1 <= 7;           -- 7 : decimal integer;  
Q2 <= "1001";     -- "1001" : 4 bit std_logic vector
```



```
.....  
Q2 <= 9;          -- 9 : decimal integer
```

... ..

**end** behavior;

# The Architecture body - General Format

```
Entity entity_name is port ( ... .. );  
End   entity_name;
```

**Architecture must be associated with entity**

```
ARCHITECTURE architecture_name of entity_name is
```


```
signal ai, bi : std_logic;
```

**Architecture declaration section: declare internal signals ( nets )**

```
BEGIN
```

```
ai <= a;  
bi <= b;  
y <= (ai AND bi);  
z <= (ai OR bi);  
x <= '1';  
w <= "1010";
```

```
END architecture_name;
```

 

# Entity / Architecture / Libraries - example

- Every design has an ENTITY/ARCHITECTURE pair

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
USE ieee.std_logic_unsigned.ALL;
```

```
ENTITY logic is
```

```
    PORT ( a,b :    IN std_logic;
```

```
           z, x, y: OUT std_logic;
```

```
           w:      OUT std_logic_vector (3 downto 0));
```

```
END logic;
```

```
ARCHITECTURE behavior of logic is
```

```
    signal ai, bi : std_logic;
```

```
BEGIN
```

```
    ai <= a;
```

```
    bi <= b;
```


```
    y <= (ai AND bi);
```

```
    z <= (ai OR bi);
```

```
    x <= '1';
```


```
    w <= "1010";
```

```
END behavior;
```

 

© LATTICE SEMICONDUCTOR CORPORATION 1998

# Libraries

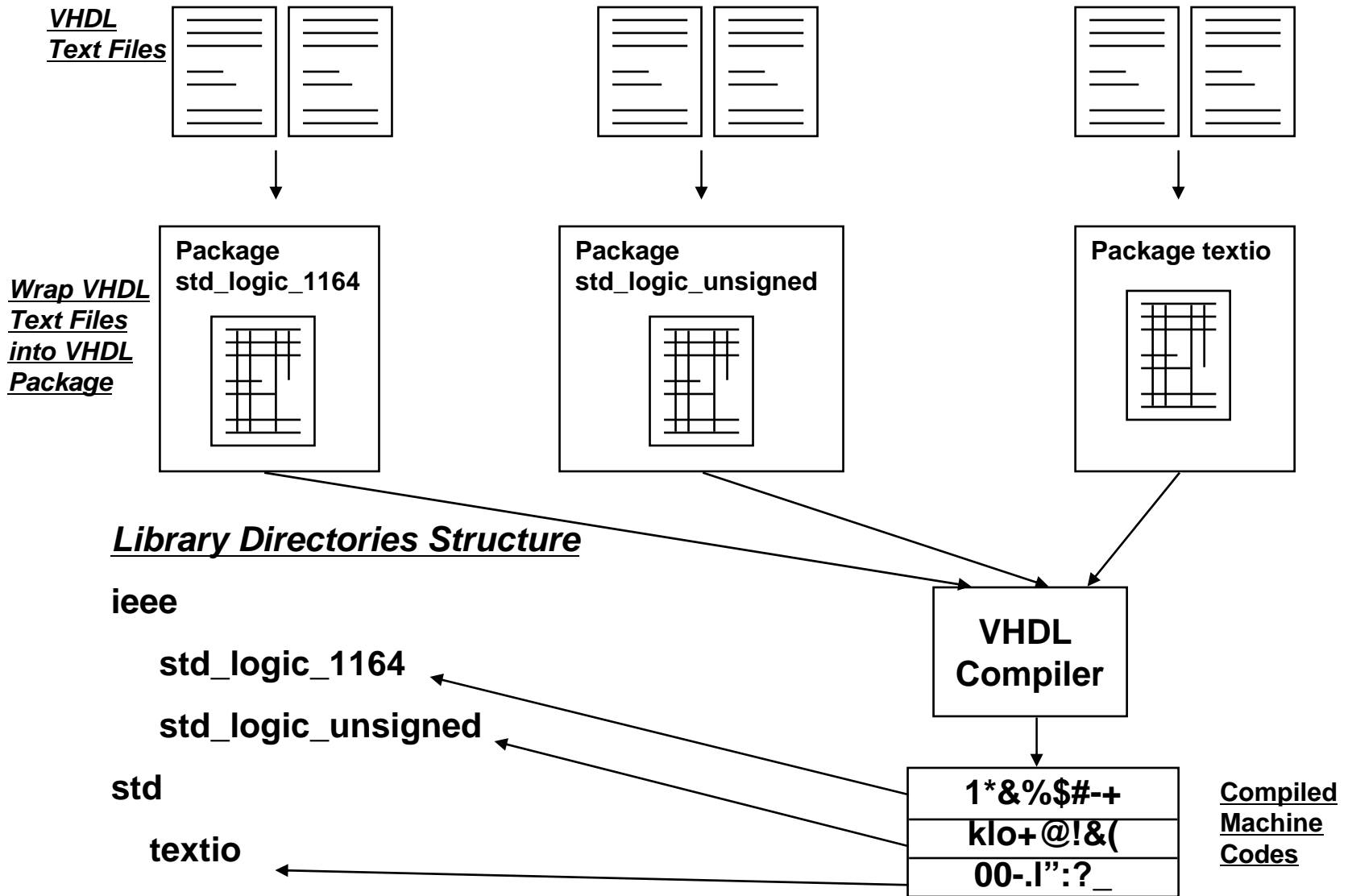

© LATTICE SEMICONDUCTOR CORPORATION 1998

# Libraries

---

- Library is a place to keep *precompiled packages* so that they can be used in other VHDL designs

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE ieee.std_logic_unsigned.ALL;
```

**ieee** - symbolic name for IEEE standard library.  
Contains packages `std_logic_1164`,  
`std_logic_unsigned`, etc.

**std\_logic\_1164** - name of the VHDL package  
Package `std_logic_1164` contains declaration  
of data type for `std_logic` and  
`std_logic_vector`.

**std\_logic\_unsigned** - name of the VHDL package.  
Package `std_logic_unsigned` contains the  
declaration of operators, functions for  
`std_logic` and `std_logic_vector` arithmetic  
operations.


# Libraries

```
LIBRARY ieee;  
-- Makes Library ieee visible  
-- to the following VHDL design.  
USE ieee.std_logic_1164.ALL;  
-- Indicates design can use all  
-- declarations of Package  
-- std_loigc_1164 in library ieee.  
USE ieee.std_logic_unsigned.ALL;
```

## Library Directories Structure

ieee

std\_logic\_1164

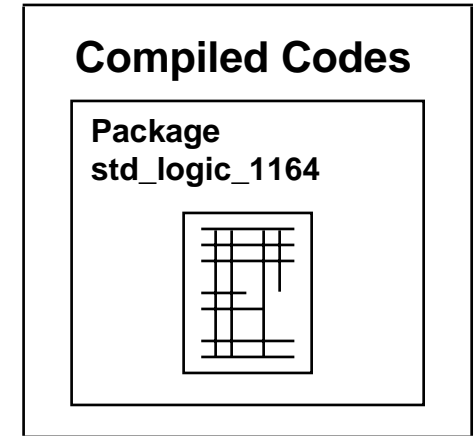

std\_logic\_unsigned

... ..

```
ENTITY design is Port  
    ( q : OUT std_logic; ... )  
End design;  
architecture context of design is  
begin  
    q <= a + b; ... ..  
End context;
```

© LATTICE SEMICONDUCTOR CORPORATION 1998

---

# VHDL Language Syntax & VHDL Design Methods

© LATTICE SEMICONDUCTOR CORPORATION 1998

FAE Training  
VHDL Training  
February 2000 15

**LATTICE PROPRIETARY**



# Concurrent Statement

Instantiation Statement  $\longrightarrow$  Structural Modeling


```
Architecture structural_modeling of one_bit_half_adder is  
begin
```

```
    X1: XOR2 Port Map ( Z0 => sum,  A0 => a,  A1 => b );
```


```
    A1: AND2 Port Map ( Z0 => cout, A0 => a,  A1 => b );
```

```
    -- A1: AND2 Port Map (      cout,      a,      b );
```

```
end structural_modeling;
```

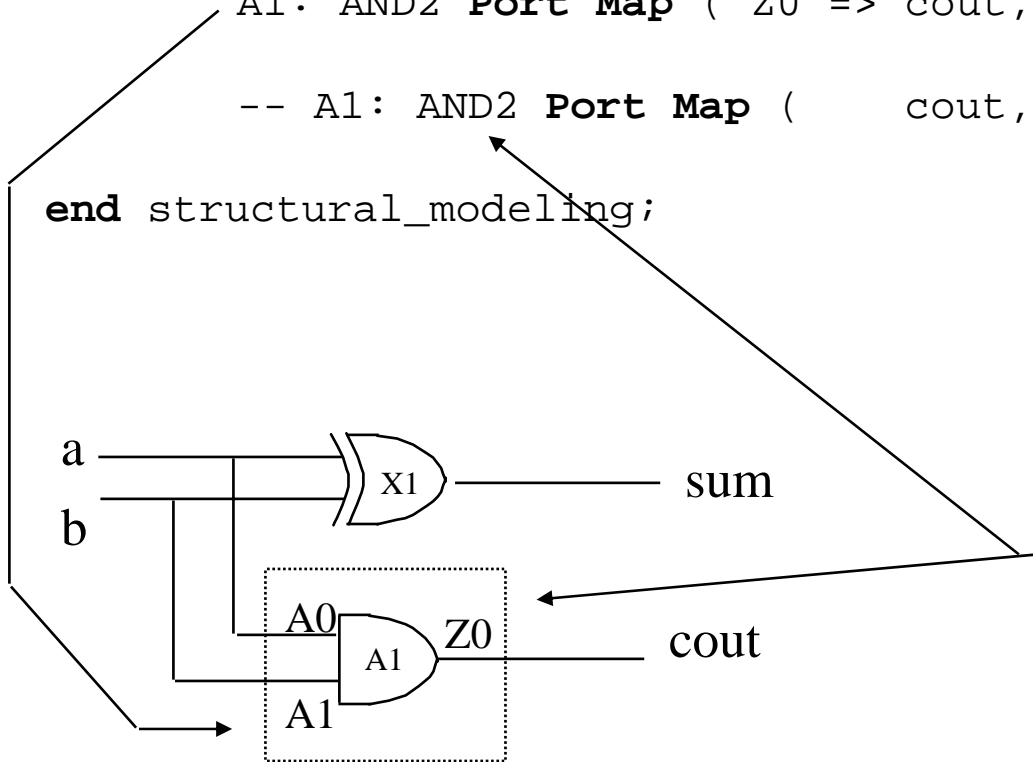

Library Symbol: AND2

 


```
Entity AND2 is Port (  
    Z0 : out std_logic;  
    A0 : in  std_logic;  
    A1 : in  std_logic );  
END AND2;
```


 
# Concurrent Statement


- Dataflow Modeling by

- boolean equations assignments
- conditional assignments (When-Else, With-Select-When)




Architecture dataflow\_modeling of example is
 
```
signal n1, n2, n3 : std_logic; -- Declare Internal Nets
begin
  x <= n2 OR n3;           n2 <= b AND sell;
  n3 <= n1 AND a;         n1 <= NOT sell;
  -- x <= (a AND (NOT sell)) OR (b AND sell);
end example;
```



# Concurrent Statement - Boolean Equation Assignment

- **Boolean Equation Assignment Format**

 

The ‘<=’ operation is also used to signify ‘taking on the value of’

- **Concatenate Assignment**

c <= a(2 downto 0) & b(3 downto 0);

c(6) <= a(2); c(5) <= a(1); c(4) <= a(0);

c(3) <= b(3); c(2) <= b(2); c(1) <= b(1); c(0) <= b(0);

# Standard VHDL Operators

---

- **Logical Operators**


AND

OR

XOR

NOT

*Boolean "True" or "False"*

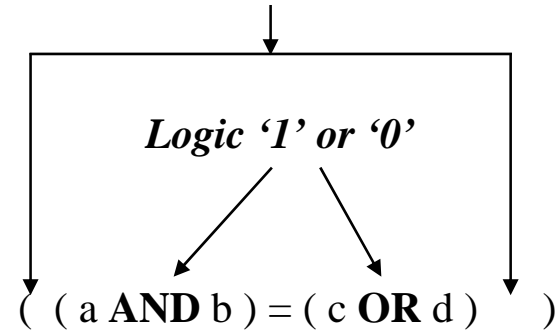

*a, b, c, d : std\_logic*

- **Relational Operators**

= Equal to

/= Not equal to

> Greater than

< Less than

>= Greater than or equal to

<= Less than or equal to

# Concurrent Conditional Assignment

- With-Select-When
- Example


```
entity mux is port (  
    a, b, c, d:in std_logic;  
    s:      in std_logic_vector(1 downto 0);  
    x:      out std_logic );  
end mux;
```

```
architecture archmux of mux is  
begin
```

```
    with s select
```

```
        x <= a when "00",      -- x is assigned based on s  
           b when "01",  
           c when "10",  
           d when "11";
```

```
end archmux;
```

 

# Concurrent conditional Assignment

---


- When-Else
- Same example of 4-to-1 mux

```
architecture archmux of mux is
```

```
begin
```

```
    x <= a when ( s = "00" ) else  
        b when ( s = "01" ) else  
        c when ( s = "10" ) else  
        d;
```

```
end archmux;
```

 

- WITH-SELECT-WHEN must specify **all mutually exclusive conditions**
- WHEN-ELSE does not have to

# With-Select-When vs. WHEN-ELSE

```
with s select
  x <= a when "00" ,
            b when "01" ,
            c when "10" ,
            d when "11" ;
```

*Specify chose values based  
on data type of "S"*

```
x <= a when ( s = "00" ) else
            b when ( s = "01" ) else
            c when ( s = "10" ) else
            d;
```

*Specify Boolean conditions*

- **Specify all mutual exclusive conditions**
- **Don't have to specify all mutually exclusive conditions, the last one can be defaulted after "ELSE" keyword**

# Sequential Statements

---


- **Process Statement** → *Behavioral Modeling*
- A PROCESS is used to describe sequential events and is included in the ARCHITECTURE of the design.
- An ARCHITECTURE can contain several PROCESS statements.
- PROCESS statements have 3 parts:
  - ❑ **Sensitivity list** :
    - includes signals used in the PROCESS
    - process is active when a signal in sensitivity list changes value
  - ❑ **PROCESS** :
    - the description of behavior
  - ❑ **BEGIN - END PROCESS** statement:
    - describes the beginning & ending of the PROCESS

# Process - Sequential Statement

- Simple example of PROCESS

```
mux: PROCESS (a, b, s) -- the sensitivity list
BEGIN
    if ( s = '0' ) then
        x <= a;
    else
        x <= b;
    end if;
END PROCESS mux;
```

-- define the process section

 

- Here the process 'mux' is sensitive to signals 'a', 'b' and 's'. Whenever signal 'a' or 'b' or 's' changes value, the statements inside the process will be evaluated




# IF - THEN - ELSE

---

- It is a sequential statement and can only be used in PROCESS
- To select a specific execution path based on Boolean evaluation of a condition or set of conditions
- Cascaded If-Then-Else
 
```
PROCESS (select, a, b, c, d)
BEGIN
    if (select = "00") then
        step <= a;
    elsif (select = "01") then
        step <= b;
    elsif (select = "10") then
        step <= c;
    else
        step <= d;
    end if;
END PROCESS;
```




- **ELSIF** allows multiple conditions in one statement
- **Must have an “END IF” statement for every “IF” statement**
 
# IF - THEN - ELSE

- Nested If-Then-Else

```
PROCESS (select, a, b, c, d)
BEGIN
  if (select = "00") then
    step <= a;
  else
    if (select = "01") then
      step <= b;
    else
      if (select = "10") then
        step <= c;
      else
        step <= d;
      end if;
    end if;
  end if;
END PROCESS;
```



# CASE - WHEN

---

- It is a sequential statement and can only be used in PROCESS

```
ARCHITECTURE archdesign OF design IS
```

```
BEGIN
```

```
    decode: PROCESS (a, b, c, option)
```

```
    BEGIN
```

```
        CASE option IS
```

```
            WHEN "00" => output <= a;
```

```
            WHEN "01" => output <= b;
```

```
            WHEN "10" => output <= c;
```

```
            WHEN OTHERS => output <= '0';
```

```
        END CASE;
```

```
    END PROCESS decode;
```

```
END archdesign;
```

- **OTHERS** is all other possible value for signals of type std\_logic

- SIGNAL
  - ❑ used to declare internal signals; not external signals
  - ❑ interconnects components
  - ❑ may be assigned to an external signal

**ARCHITECTURE** behavior of example is

```
SIGNAL count:      std_logic_vector (3 downto 0);  
SIGNAL flag:       integer;  
SIGNAL mtag:       integer range 0 to 15;  
SIGNAL stag:       integer range 100 downto 0;
```

**BEGIN**

```
--mtag is a 4-bit array; MSB is mtag(0); LSB is mtag(3)  
--stag is a 7-bit array; MSB is stag(6); LSB is stag(0)  
--always declared in ARCHITECTURE section
```


# Data Objects

- SIGNAL in User-defined enumeration type

□ represents state elements in a state-machine

**ARCHITECTURE** behavior of example is
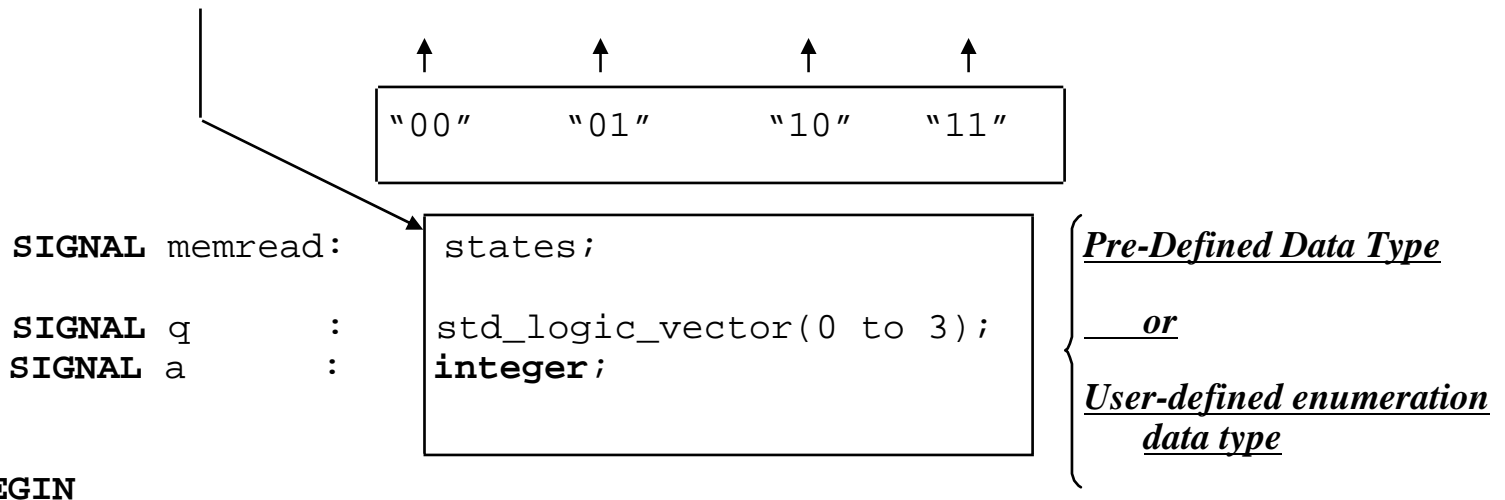
```
TYPE states is (state0, state1, state2, state3);
```



**BEGIN**

```
--each state (state0, state1, etc) represents a distinct state.
```

# Data Objects

---

- CONSTANT

- holds a specific value of a type that cannot be changed within the design description

**ARCHITECTURE** behavior of example is

```
    CONSTANT width: integer := 8;
```

```
BEGIN
```

```
-- "width" is a constant with integer type and has a value of "8"
```

- VARIABLE

- used to declare local values only within a given PROCESS.

```
PROCESS (s)
```

```
    VARIABLE result: integer := 12;
```

```
BEGIN
```

```
-- "result" is a VARIABLE with an initial value of "12".
```

```
-- value of "result" may be modified within a PROCESS.
```

- |  |                    |
|--|--------------------|
| <ul style="list-style-type: none"><li>• variable assignment use</li></ul>    | <code>:=</code>    |
| <ul style="list-style-type: none"><li>• port/signal assignment use</li></ul> | <code>&lt;=</code> |

---

# Understand VHDL Synthesis and VHDL Design Application

© LATTICE SEMICONDUCTOR CORPORATION 1998

FAE Training  
VHDL Training  
February 2000 31

**LATTICE PROPRIETARY**



# REGISTERS in Behavioral VHDL

- 3 ways to describe a register

```
❑ PROCESS (clk)
```

```
  BEGIN
```


```
    IF (clk'event and clk='1') THEN -- rising edge of clk
```

```
      q <= d;
```

```
    END IF;
```

```
  END PROCESS;
```
 
```
-- falling edge of clk => (clk'event and clk = '0')
```



```
❑ PROCESS (clk)
```


```
  BEGIN
```

```
    IF RISING_EDGE (clk) THEN
```

```
      q <= d;
```

```
    END IF;
```

```
  END PROCESS;
```

 

```
❑ PROCESS -- no sensitivity list
```

```
  BEGIN
```

```
    WAIT UNTIL clk'event AND clk = '1';
```

```
      q <= d;
```

```
  END PROCESS;
```



# Synchronous/Asynchronous Reset Register

---

**ARCHITECTURE** behavior of synchronous\_reset\_register is  
**BEGIN**

```
PROCESS (clk)
BEGIN
    IF (clk'EVENT and clk = '1') then
        IF (rst = '1') then
            q <= '0';
        ELSE
            q <= d;
        END IF;
    END IF;
END PROCESS;
```

**END** behavior;


**ARCHITECTURE** behavior of Asynchronous\_reset\_register is  
**BEGIN**

```
PROCESS (rst, clk)
BEGIN
    IF (rst = '1') then
        q <= '0';
    ELSIF (clk'EVENT and clk = '1') then
        q <= d;
    END IF;
END PROCESS;
```

**END** behavior;
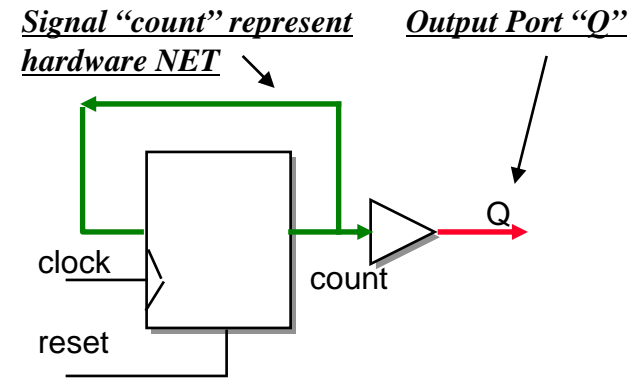
# Synchronous Reset Counter

```
Entity counter is
  port (clock : IN std_logic;
        reset : IN std_logic;
        Q: OUT std_logic_vector(3 downto 0));
End counter;
```



Architecture behavior of counter is

```
  signal count : std_logic_vector(3 downto 0);
begin
  upcount: PROCESS (clock)
  BEGIN
    IF (clock'EVENT AND clock = '1') THEN
      IF reset = '1' THEN
        count <= "0000"; -- synchronous
      ELSE
        count <= count + "0001";
      END IF;
    END IF;
  END PROCESS upcount;
  Q <= count;
```

End behavior;

# Asynchronous Reset Counter

**Entity** counter **is**


```
port (clock, reset : IN std_logic;  
      count: buffer std_logic_vector(3 downto 0));
```

**End** counter;

**Architecture** behavior **of** counter **is**

```
begin upcount: PROCESS (clock, reset)  
  BEGIN IF (reset = '1') THEN  
    -- reset has a higher priority  
    count <= "0000"; -- asynchronous  
  ELSIF (clock'EVENT AND clock = '1') THEN  
    count <= count + "0001";  
  END IF;  
END PROCESS upcount;
```

**End** behavior;

 


# LATCHES - in Behavioral VHDL

---


ARCHITECTURE behavior of d\_latch is
 
```
BEGIN
  PROCESS (enable)
  BEGIN
    IF (enable = '1') then
      outa <= ina;
    END IF;
  END PROCESS;
END behavior;
```



ARCHITECTURE behavior of set\_reset\_latch is
 
```
BEGIN
  PROCESS (set, reset)
  BEGIN
    IF (set = '1' AND reset = '0') then
      outa <= '1';
    ELSIF (set = '0' AND reset = '1') then
      outa <= '0';
    END IF;
  END PROCESS;
END behavior;
```



# Synchronous/Asynchronous Reset Latch

---

**ARCHITECTURE** behavior of synchronous\_reset\_d\_latch is  
**BEGIN**

```
PROCESS (enable)
BEGIN
  IF (enable = '1') then
    IF ( rst = '1') then
      outa <= '0';
    ELSE
      outa <= ina;
    END IF;
  END IF;
END PROCESS;
```

**END** behavior;

**ARCHITECTURE** behavior of asynchronous\_reset\_d\_latch is  
**BEGIN**

```
PROCESS (enable, rst)
BEGIN
  IF (rst = '1') then
    outa <= '0';
  ELSIF (enable = '1') then
    outa <= ina;
  END IF;
END PROCESS;
```

**END** behavior;

# Output Enables

---

```
Entity design is port ( q : out std_logic_vector(0 to 6); ...);  
End design;      -- Tri-State Port declared as OUT
```

ARCHITECTURE behavioral of design is

BEGIN

```
q <= qint when (oe='1') else "ZZZZZZZ" ;
```

END behavioral;

ARCHITECTURE behavioral of design is

BEGIN

PROCESS (oe)

```
BEGIN if ( oe = '1' ) then
```

```
    q <= qint;
```


```
else
```

```
    q <= "ZZZZZZZ";
```

```
end if;
```

END PROCESS;

END behavioral;

 

# Bi-Directional Port

Entity design is port(-- Bi-Directional Port declared as INOUT

```
data: inout std_logic_vector(0 to 7);...);
```

```
End design;
```

```
ARCHITECTURE behavior OF design IS
```

```
SIGNAL ext_input : std_logic;
```

```
BEGIN
```

```
data <= count WHEN oe = '1' ELSE "ZZZZZZZZ" ;
```

```
ext_input <= data;
```

```
END behavior;
```

```
ARCHITECTURE behavior OF design IS
```

```
SIGNAL ext_input : std_logic;
```

```
BEGIN
```

```
PROCESS (oe)
```

```
BEGIN
```

```
IF (oe = '1' ) THEN
```

```
data <= count;
```

```
ELSE
```


```
data <= "ZZZZZZZZ";
```

```
END IF;
```

```
END PROCESS;
```

```
ext_input <= data;
```


```
END behavior;
```

 
 
# CPLD Optimization - Caution using “If-Then-Else”


- The following VHDL file does not specify the value of “q” when “a1” is equal to “0”, thus creating a “Latch”.

```
PROCESS (a1, d)
BEGIN
    IF (a1 = '1') then
        q <= d;
    END if;
END PROCESS;
```



- The following VHDL file specifies the value of “q” when “a1” is equal to “0”, thus creating an AND gate
 
```
PROCESS (a1, d)
BEGIN
    IF (a1 = '1') then
        q <= d;
    ELSE
        q <= '0';
    END if;
END PROCESS;
```





# CPLD Optimization - Caution using “Case-When”

- This VHDL file generates unwanted latches because not all states are defined.

```
signal sel:std_logic_vector(0 to 1);
```

```
PROCESS (sel,a,b)
BEGIN
  CASE sel IS
    WHEN "00"=>q<=a;
    WHEN "11"=>q<=b;
  END CASE;
END PROCESS;
```

- This VHDL file generates a multiplexer correctly because states “10” and “01” are defined.


```
-- sel can choose either of
"00","01","10","11"
```

```
PROCESS (sel,a,b)
BEGIN
  CASE sel IS
    WHEN "00"=>q<=a;
    WHEN "11"=>q<=b;
    WHEN OTHERS=>q<='0';
  END CASE;
END PROCESS;
```

# CPLD Optimization - Use of Parentheses

 
- Example listing below generates a design that uses three cascaded adders and three logic levels.

```
PROCESS (a,b,c,d)
BEGIN
    sum<=a+b+c+d;
END PROCESS;
```



 - Example listing below, by inclusion of two sets of parentheses, generates two parallel adders whose outputs the circuit then adds. This design results in two logic levels.

```
PROCESS (a,b,c,d)
BEGIN
    sum<=(a+b)+(c+d);
END PROCESS;
```



---

# VHDL Hierarchical Design

© LATTICE SEMICONDUCTOR CORPORATION 1998

FAE Training  
VHDL Training  
February 2000 43

**LATTICE PROPRIETARY**




# Concept of Hierarchical Design
 
## Low-level Design

```
ENTITY tff is port
  (d, clk, rst : in std_logic; q : out std_logic);
end tff;


ARCHITECTURE context of tff is begin
  D_FF:          FD21 port map(d, q, clk, rst);
  NOT_Gate:      INV  port map(d, q);
end context;
```


 
## High-Level Design

```
ENTITY ripple_counter is port
  (cnt_en, clk, rst : in std_logic; q : out std_logic );
end ripple_counter;

ARCHITECTURE structure of
  ripple_counter is
BEGIN
  tff0 : tff port map (...);
  tff1 : tff port map (...);
  tff2 : tff port map (...);
  tff3 : tff port map (...);
end structure;
```



# COMPONENT

- Top level example

```
ENTITY addmult is
    port(    sig1,sig2: in  std_logic_vector(0 to 3);
           result: out std_logic_vector(0 to 7));
end addmult;
```

```
ARCHITECTURE structure of addmult is
    SIGNAL s_add: std_logic_vector(0 to 7);
```

```
COMPONENT add    -- component declaration
    port(op1,op2: in std_logic_vector(0 to 3);
          ret: out std_logic_vector(0 to 7));
end component;
```

```
                                --component instantiation
                                --name of lower level component
                                --key word connecting two levels
BEGIN
    add1: add port map(op1=>sig1, op2=>sig2, ret=>s_add);

    result <= s_add - "00000001";
end structure;
```

Top Level: **Addmult**  
component declaration:  
**Add** ←  
Instantiation of component

Low Level:  
**Add**

# COMPONENT (cont.)

- Top level design contains component declaration

```
COMPONENT add
    port(op1,op2: in std_logic_vector(0 to 3));
        ret: out std_logic_vector(0 to 7));
end component;
```

Component name identical to entity name in low-level design.

- Lower level design of previous example

```
ENTITY add is
    PORT(op1,op2: in std_logic_vector(0 to 3));
        ret: out std_logic_vector(0 to 7));
end add;
ARCHITECTURE dataflow of add is
BEGIN
    ret <= op1 + op2;
end dataflow;
```

port declaration in component and low-level entity are identical.

- Lower level design can be in a separate file or in the same file as the top-level design